

# ANALOG CIRCUITS

Complete Multipage Master Handbook & Problem Solver | GATE ECE 2027

---

|                       |                                                   |
|-----------------------|---------------------------------------------------|
| Target Exam:          | GATE 2027 Electronics & Communication (EC)        |
| Organizing Institute: | IIT Madras                                        |
| Syllabus Standard:    | 100% Complete Syllabus + 2027 Revisions           |
| Edition:              | Comprehensive Multipage Textbook & Problem Solver |

## TABLE OF CONTENTS

---

|                                                                   |        |
|-------------------------------------------------------------------|--------|
| <b>Chapter 1:</b> Diode Circuits & Regulators                     | Page 3 |
| <b>Chapter 2:</b> BJT & MOSFET Small-Signal Amplifiers            | Page 4 |
| <b>Chapter 3:</b> Op-Amp Circuits & Active Filters                | Page 5 |
| <b>Chapter 4:</b> Op-Amp Frequency Response & Miller Compensation | Page 6 |
| <b>Chapter 5:</b> Feedback Amplifiers & Oscillators               | Page 7 |

# CHAPTER 1: DIODE CIRCUITS & REGULATORS

---

## 1.1 Shockley Equation, Rectifiers & Clampers

Diodes act as non-linear unidirectional switches.

- **Diode Dynamic Resistance:**  $r_d = V_T / I_D$ .
- **Clamper Circuit:** Preserves peak-to-peak voltage  $V_{p-p}$  while shifting DC level.

## CHAPTER 2: BJT & MOSFET SMALL-SIGNAL AMPLIFIERS

---

### 2.1 Hybrid-pi Model & Small-Signal Gain

Transistors are biased in active/saturation region for linear amplification.

- **BJT Transconductance:**  $g_m = I_C / V_T$ .
- **MOSFET Saturation Current:**  $I_D = (1/2) * \mu_n * C_{ox} * (W/L) * (V_{GS} - V_{th})^2$ .

## CHAPTER 3: OP-AMP CIRCUITS & ACTIVE FILTERS

---

### 3.1 Ideal Op-Amp Rules & Applications

Ideal Op-Amps operate under infinite gain and zero input current rules.


- **Virtual Short:**  $V_+ = V_-$  under negative feedback.
- **Inverting Gain:**  $A_v = -R_f / R_1$ .
- **Non-Inverting Gain:**  $A_v = 1 + R_f / R_1$ .

## CHAPTER 4: OP-AMP FREQUENCY RESPONSE & MILLER COMPENSATION
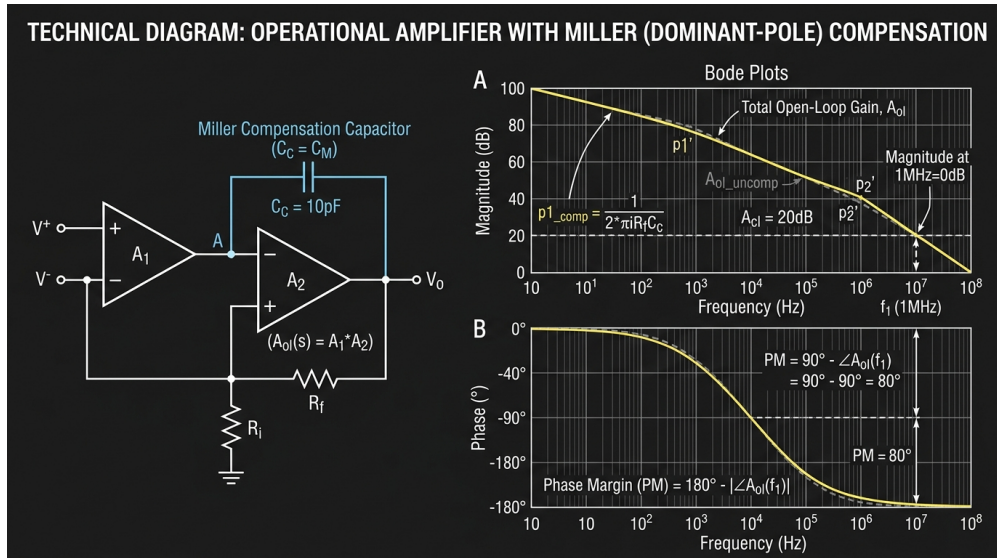
### 4.1 Miller (Dominant-Pole) Compensation & Phase Margin (NEW FOR GATE 2027)

Miller compensation stabilizes feedback amplifiers by pole splitting.

- **Pole Splitting:** Dominant pole  $p_1$  moves to lower frequency  $p_1' = 1/(2\pi R_{in} A_2 C_C)$ .
- **Gain-Bandwidth Product:**  $GBW = g_{m1} / (2\pi C_C)$ .
- **Phase Margin:**  $PM = 180^\circ + \angle(T(j\omega_{gc}))$ . Target  $PM \geq 60^\circ$  for clean stability.



#### WORKED GATE NUMERICAL: Miller Capacitor Calculation

**Problem:** Find Miller capacitor  $C_C$  for  $GBW = 10\text{ MHz}$  given  $g_{m1} = 0.628\text{ mA/V}$ .

**Step-by-Step Derivation & Solution:**

$$GBW = g_{m1} / (2\pi C_C) \rightarrow C_C = 0.628 \times 10^{-3} / (2\pi \times 10^7) = 10\text{ pF}.$$

## CHAPTER 5: FEEDBACK AMPLIFIERS & OSCILLATORS

---

### 5.1 4 Feedback Topologies & Barkhausen Criterion

Feedback alters input and output impedances and stability.

- **Voltage-Series Feedback:** Increases  $R_{in}$ , decreases  $R_{out}$ .
- **Barkhausen Condition:**  $|A * \beta| = 1$  and phase shift angle( $A * \beta$ ) =  $0^\circ$  or  $360^\circ$  for sustained oscillation.